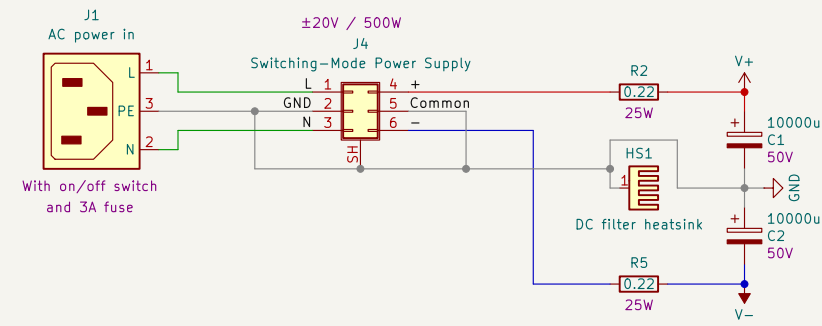
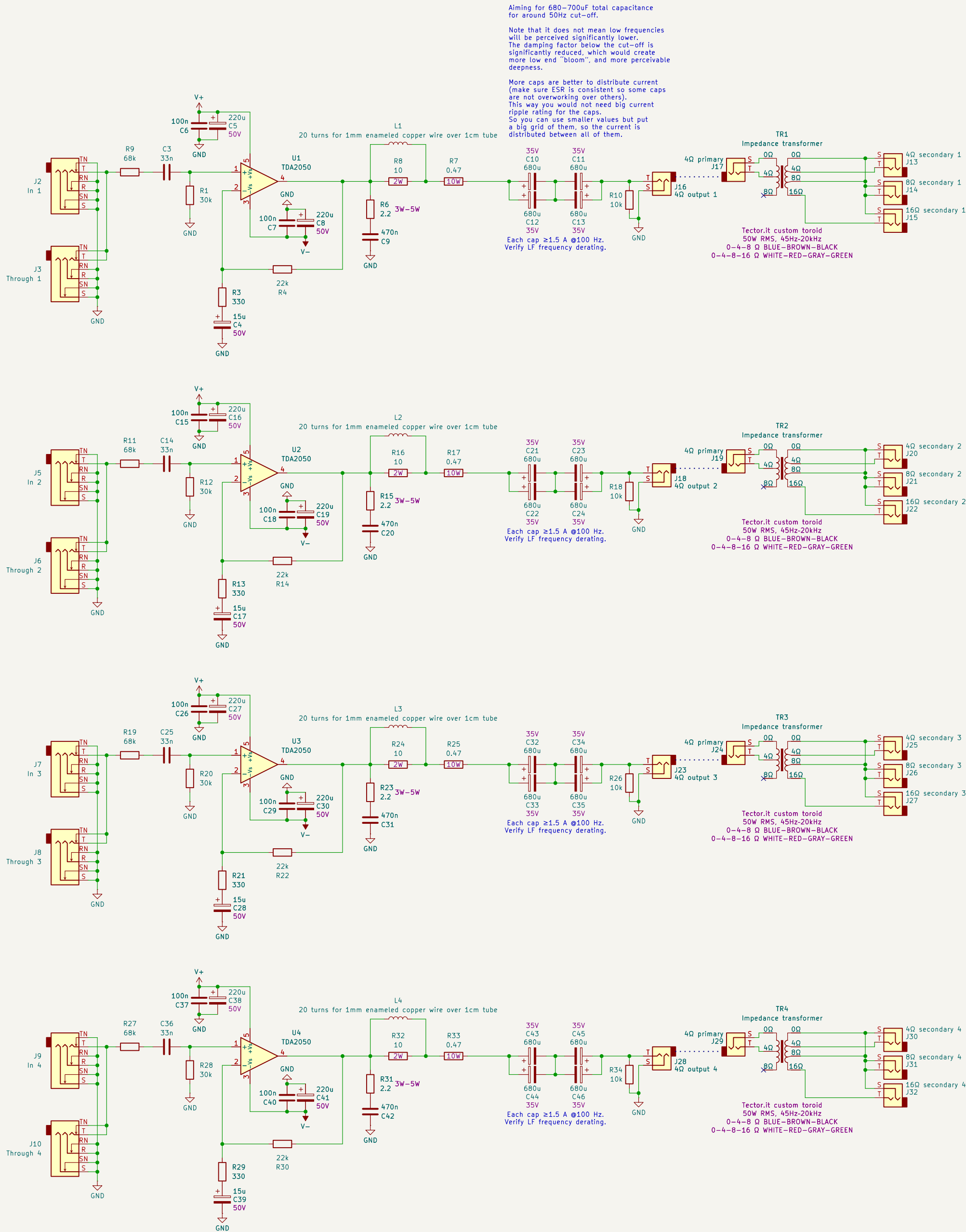




You should expect around 30W of power for each amplifier channel into 4 ohms. The idea is that all 4 are driving 4 speakers independently, so that you get enough power, while each individual amps is not that powerful.

Everything is designed around 4 ohms load. The impedance transformers are supposed to keep that 4 ohms load consistency regardless of actual speaker load you connect it to.

Mind that older TDA2050 chips seem to be rated for lower voltages, so that's why I picked $\pm 20V$ supply, because it seems I have the older model. Otherwise you could power it from $\pm 24V$ for more output power, more headroom. Also be aware that TDA2050 is obsolete, no longer manufactured, there are a lot of fakes in the market.